



# COE 328 - Lab 2

## Prelab

### 2 Pre-Lab Preparation

Implementation of the simple logic functions with NAND gates

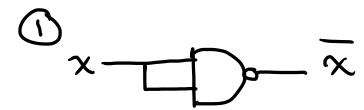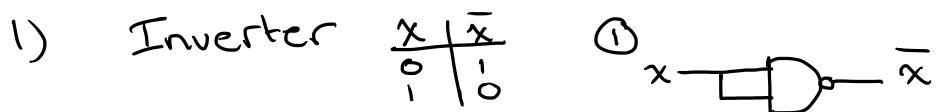1. Determine 2 ways to implement an inverter with a 2-input NAND gate.
2. Implement a 3-input NAND gate function using 2-input NAND gates only, draw schematics.
3. Implement a 2-input OR function using 2-input NAND gates only, draw schematics.
4. (A) Implement the function  $Z = f(A, B) = (A + B)\overline{AB}$  using one 2-input OR gate, one 2-input AND gate and one 2-input NAND gate.  
(B) Implement the same function  $Z$  with only NAND gates.  
(C) Make up the truth table for the function. What is the common name of this function?  
(D) Expand and simplify the Boolean equation to express  $Z$  as a sum of products. Implement the sum of products using only NAND gates. Note: It is possible to do so with 4 NAND gates and no additional inverters.



2)

$x_1$	$x_2$	$x_3$	$f$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

$$f = \underbrace{\bar{x}_1 + \bar{x}_2}_{K} + \bar{x}_3$$

general function of NAND  
 $= \overline{x_1 x_2}$


$$K = \overline{x_1 + x_2}$$

$$\bar{K} = \overline{x_1 x_2}$$

$$f = K + \bar{x}_3$$

$$\bar{f} = \overline{K + x_3}$$

$$f = \overline{\bar{K} \cdot x_3}$$

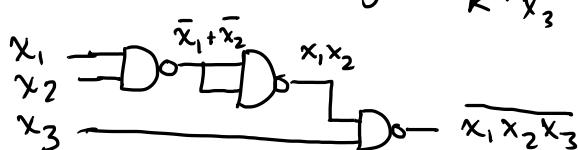


3)

$x_1$	$x_2$	$f$
0	0	0
0	1	1
1	0	1
1	1	1


$$f = x_1 + x_2$$

$$f = \overline{x_1 x_2}$$


$$= \bar{x}_1 + \bar{x}_2$$

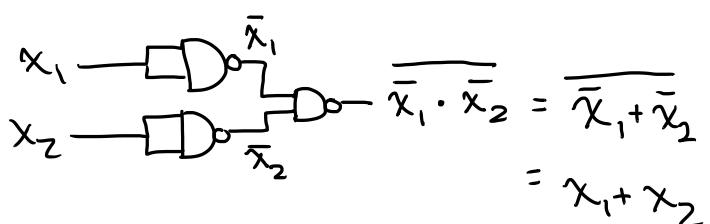

4) a)  $Z = f(A, B) = (A + B) \bar{AB}$

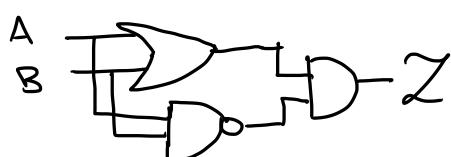

b) Only using NAND gates

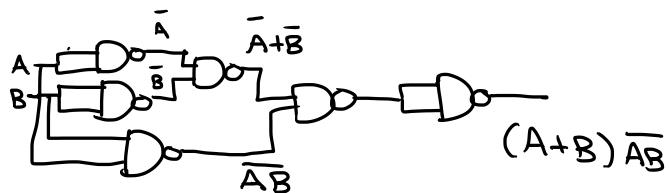

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0

XOR gate

$$\begin{aligned}
 d) \quad Z &= (A+B)\bar{AB} \\
 &= (A+B)(\bar{A}+\bar{B}) \\
 &= (\cancel{A}\bar{A} + A\bar{B} + B\bar{A} + \cancel{B}B) \\
 &= A\bar{B} + B\bar{A}
 \end{aligned}$$

