

<b>Course Title:</b>	COE
<b>Course Number:</b>	328
<b>Semester/Year (e.g.F2016)</b>	2020

<b>Instructor:</b>	
--------------------	--

<i>Assignment/Lab Number:</i>	Lab 1
<i>Assignment/Lab Title:</i>	

<i>Submission Date:</i>	
<i>Due Date:</i>	

Student LAST Name	Student FIRST Name	Student Number	Section	Signature*
Youssef	Kirolos	500968175	04	K.Y

\*By signing above you attest that you have contributed to this written lab report and confirm that all work you have contributed to this lab report is your own work. Any suspicion of copying or plagiarism in this work will result in an investigation of Academic Misconduct and may result in a "0" on the work, an "F" in the course, or possibly more severe penalties, as well as a Disciplinary Notice on your academic record under the Student Code of Academic Conduct, which can be found online at: <http://www.ryerson.ca/senate/current/pol60.pdf>

# Table of Contents

## Introduction

- Purpose of lab

## Lab work

- Figure for Block Diagram

- Figure for waveform

### Part 2

- Figure for VHDL Code

- Figure for waveform

### Part 3

- Figure For 2 VHDL Codes

- Figure for Combined block Diagram

- Figure for Waveform

## Discussion & Conclusion

- Result discussion

- Lab Take-Aways


## Introduction

### Lab Objectives


- ◇ Introduction to Quartus II software and its tools
- ◇ To design, compile and simulate block diagram schematics and VHDL-based design
- ◇ Introduction to modular design and mixed-design entry

### Lab work

#### Figure for Block Diagram

 

#### Figure for waveform

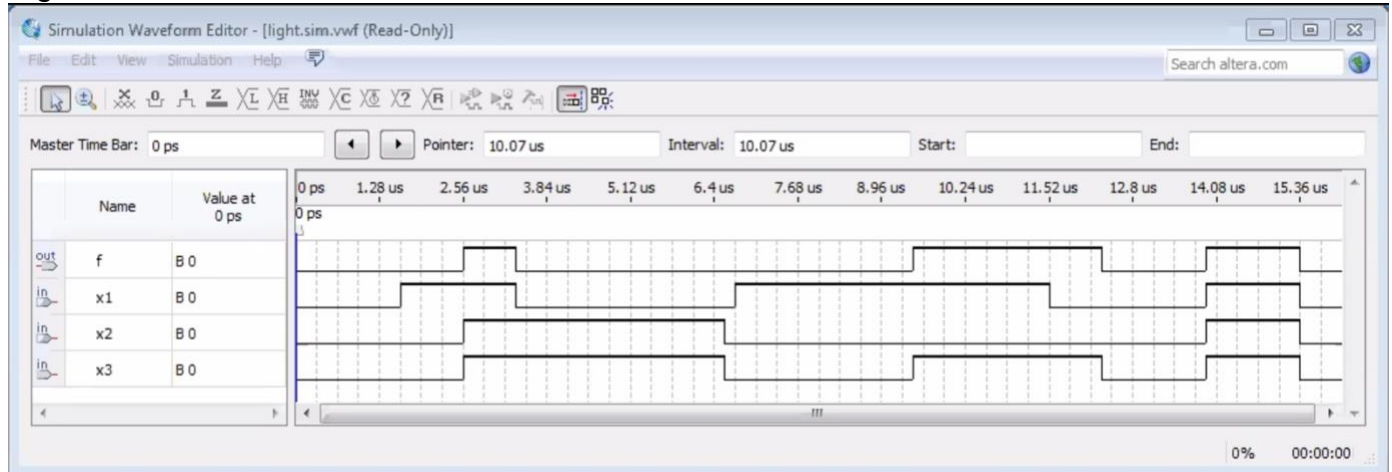

### Part 2

Figure for VHDL Code


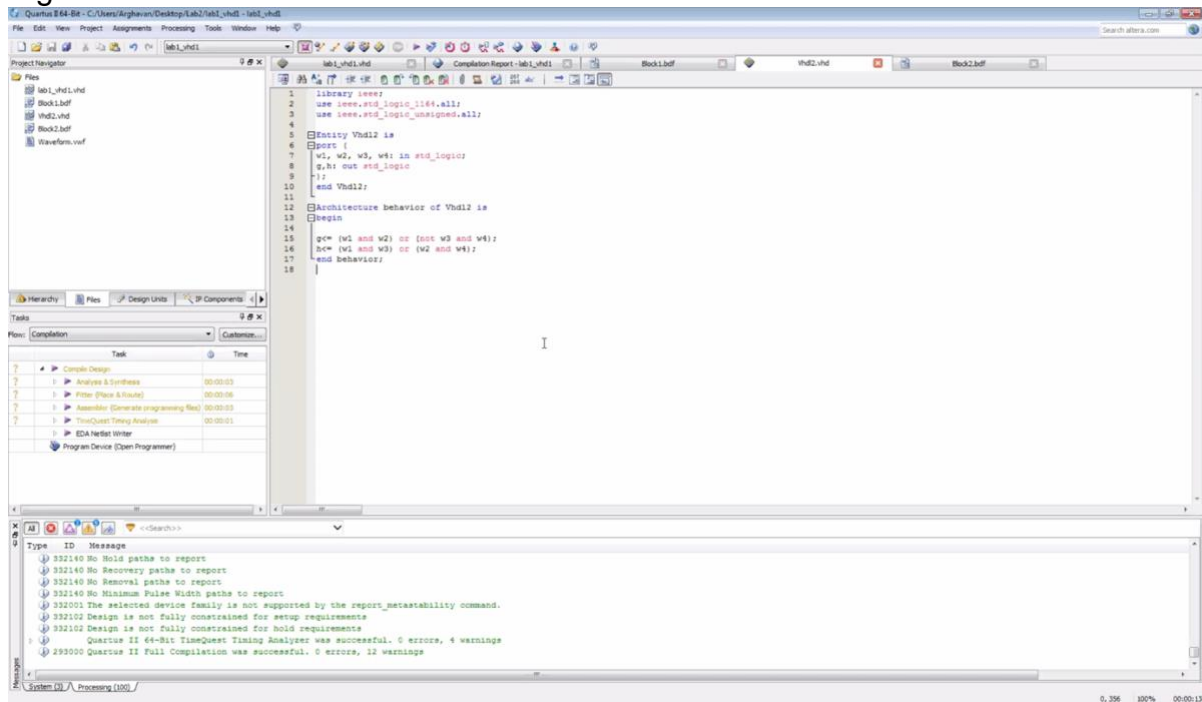


Figure for waveform

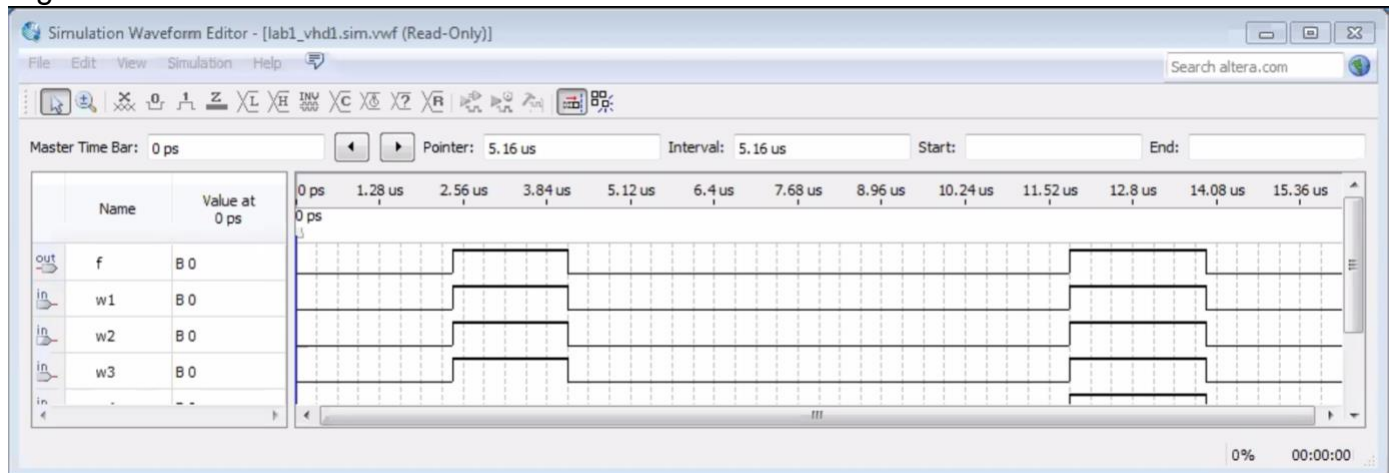

Part 3

Figure For 2 VHDL Codes

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.all;
3  USE ieee.std_logic_unsigned.all;
4
5  ENTITY lab1_vhdl1 IS
6  PORT (
7    x1,x2,x3 : IN STD_LOGIC ;
8    f : OUT STD_LOGIC );
9  end lab1_vhdl1;
10
11 ARCHITECTURE Behavior OF lab1_vhdl1 IS
12 BEGIN
13   f <= --Insert code here
14   END Behavior;
15
16

```

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.all;
3  USE ieee.std_logic_unsigned.all;
4
5  ENTITY lab1_vhdl2 IS
6  PORT (
7    w1,w2,w3,w4 : IN STD_LOGIC ;
8    g,h : OUT STD_LOGIC );
9  end lab1_vhdl2;
10
11 ARCHITECTURE Behavior OF lab1_vhdl2 IS
12 BEGIN
13   --Insert code here
14   END Behavior;
15
16
17

```

Figure for Combined block Diagram


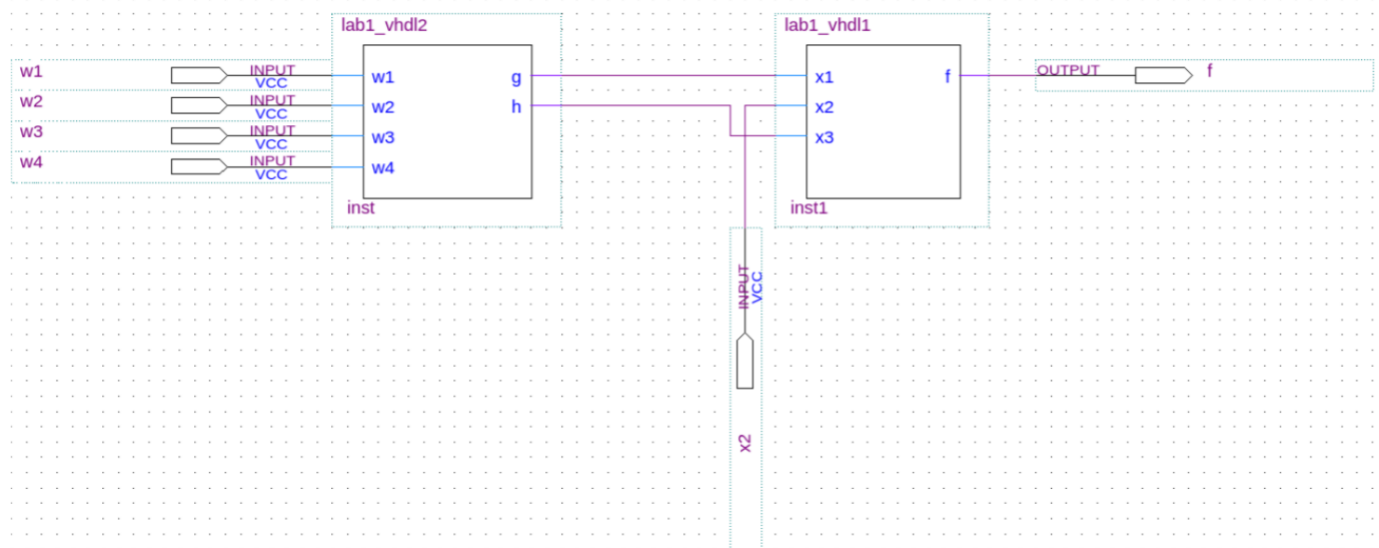


Figure for Waveform

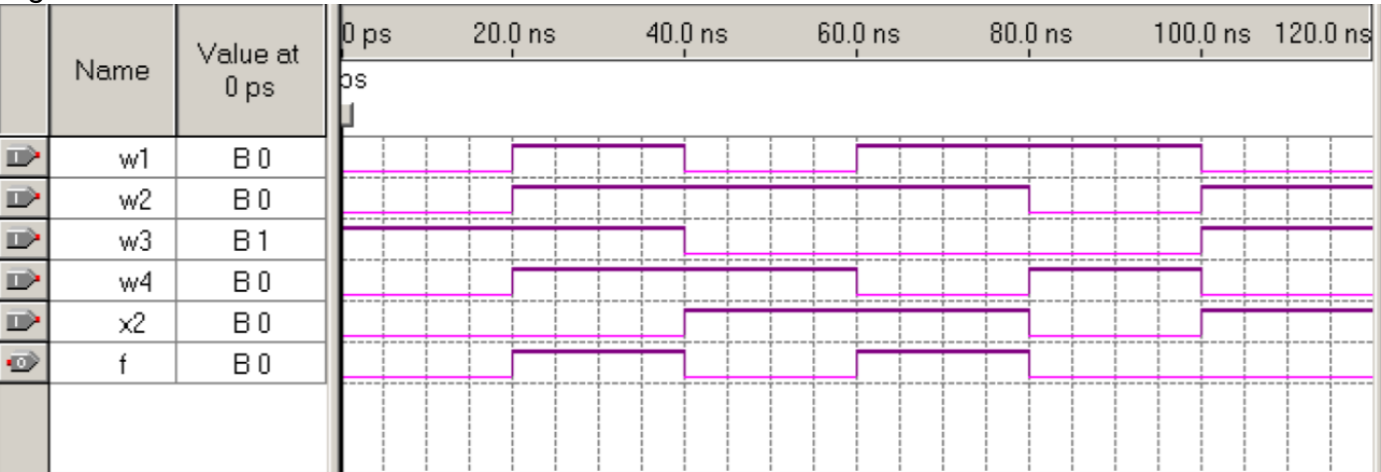

Discussion & Conclusion

The objective of this lab is to familiarize ourselves with the Quartus 2 program and the different methods of simulating and representing a circuit with logic gates.

Result discussion

The results

As expected, the waveform output represented the combination of the VHDL codes shown in the combined block diagram (a sum of product of 3 inputs) and matched the truth table.

Lab Take-Aways

Quartus is a powerful tool for simulating complex circuits that can be broken down into simpler functions in cascade and can conveniently display the output value of the circuit when the input values are manipulated.